



UNIVERSITY  
IYUNIVESITHI  
UNIVERSITEIT

# E344 Assignment 1

Daanyaal Mullah

22898220

Report submitted in partial fulfilment of the requirements of the module  
Design (E) 344 for the degree Baccalaureus in Engineering in the Department of Electrical  
and Electronic Engineering at Stellenbosch University.

July 31, 2022

## Plagiaatverklaring / Plagiarism Declaration

1. Plagiaat is die oorneem en gebruik van die idees, materiaal en ander intellektuele eiendom van ander persone asof dit jou eie werk is.

*Plagiarism is the use of ideas, material and other intellectual property of another's work and to present is as my own.*

2. Ek erken dat die pleeg van plagiaat 'n strafbare oortreding is aangesien dit 'n vorm van diefstal is.

*I agree that plagiarism is a punishable offence because it constitutes theft.*

3. Ek verstaan ook dat direkte vertalings plagiaat is.

*I also understand that direct translations are plagiarism.*

4. Dienooreenkomsdig is alle aanhalings en bydraes vanuit enige bron (ingesluit die internet) volledig verwys (erken). Ek erken dat die woordelikse aanhaal van teks sonder aanhalingsstekens (selfs al word die bron volledig erken) plagiaat is.

*Accordingly all quotations and contributions from any source whatsoever (including the internet) have been cited fully. I understand that the reproduction of text without quotation marks (even when the source is cited) is plagiarism*

5. Ek verklaar dat die werk in hierdie skryfstuk vervat, behalwe waar anders aangedui, my eie oorspronklike werk is en dat ek dit nie vantevore in die geheel of gedeeltelik ingehandig het vir bepunting in hierdie module/werkstuk of 'n ander module/werkstuk nie.

*I declare that the work contained in this assignment, except where otherwise stated, is my original work and that I have not previously (in its entirety or in part) submitted it for grading in this module/assignment or another module/assignment.*

22898220	
Studentenommer / Student number	Handtekening / Signature
D. Mullah Voorletters en van / Initials and surname	July 31, 2022 Datum / Date

# Contents

<b>Declaration</b>	i
<b>List of Figures</b>	iii
<b>List of Tables</b>	iv
<b>Nomenclature</b>	v
<b>1. Literature survey</b>	1
1.1. Operational amplifiers . . . . .	1
1.2. Current sensing . . . . .	4
<b>2. Detail design</b>	5
<b>3. Results</b>	7
3.1. Current sensor . . . . .	7
3.2. Current sensor Physical Measurements . . . . .	8
<b>Bibliography</b>	9
<b>A. Social contract</b>	10
<b>B. GitHub Activity Heatmap</b>	11

# List of Figures

1.1.	Frequency Response and Bandwidth . . . . .	2
1.2.	Voltage Follower . . . . .	2
1.3.	Inverting Amplifier . . . . .	2
1.4.	Voltage Comparator . . . . .	3
1.5.	Non-Inverting Amplifier . . . . .	3
1.6.	Lowside vs Highside . . . . .	4
1.7.	Different Current Sensors . . . . .	4
2.1.	Stalling Test . . . . .	5
2.2.	Simulation . . . . .	6
2.3.	Final Design . . . . .	6
3.1.	Circuit and Output . . . . .	7
3.2.	Input Vs Output . . . . .	7
3.3.	physical circuit . . . . .	8
3.4.	stalling test . . . . .	8
3.5.	running test . . . . .	8

# **List of Tables**

# Nomenclature

## Variables and functions

Update this list to make it applicable to your project.

- $p(x)$  Probability density function with respect to variable  $x$ .  
 $P(A)$  Probability of event  $A$  occurring.

## Acronyms and abbreviations

AC	Alternating Current
DC	Direct Current
Op-Amp	Operational Amplifier
BW	Bandwidth
R	Resistor
W	Watt
PS	Power Supply
dB	Decibel

# **Chapter 1**

## **Literature survey**

The purpose of this document is to present the reader with the basic principles low side current sensing. In order to do this, the most commonly used operational amplifiers are examined as well as the basics of current sensing. By observing the purpose and specifications of different configurations. The correct filter and operational amplifier configuration can be chosen in order to implement a low side current sensor.


### **1.1. Operational amplifiers**

#### **Operational amplifiers: limitations and considerations**


Practical operational amplifiers have certain limitations when compared to ideal operational amplifiers. For example a differential amplifier amplifies the difference between the two input terminals. Therefor ideally if the two input terminals were the same then the output should be zero. In practice though this does not happen. There will be noise at the terminals which will make the inputs unequal and even if they were equal the operational amplifier would still have an output. When designing the correct configuration, the slew rate, bandwidth, input current and common mode rejection need to be considered. When observing the circuits frequency response, we design it to obtain the correct frequency response over a specific bandwidth. All practical operational amplifiers have a finite BW, this point where the gain begins to roll-over as the frequency increases is called the '3dB point'. It is shown in figure 1.1.

#### **Operational amplifier configurations**


Using different configurations of resistors and capacitors, many different types of operational amplifiers can be made. Some of the different types include inverting amplifiers, non-inverting amplifier, voltage follower, comparator, differential, summing and integrators. Operational amplifiers can have four different types of gain. Voltage gain, voltage in is amplified making voltage out larger in magnitude. Current gain, the current is amplified. Transconductance, voltage is made into current and finally trans resistance where current in and voltage out.

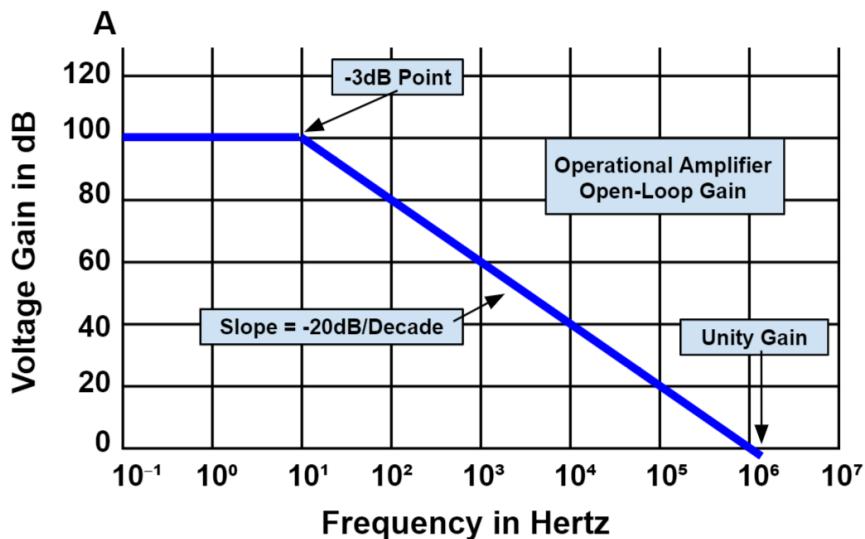


**Figure 1.1:** Frequency Response and Bandwidth

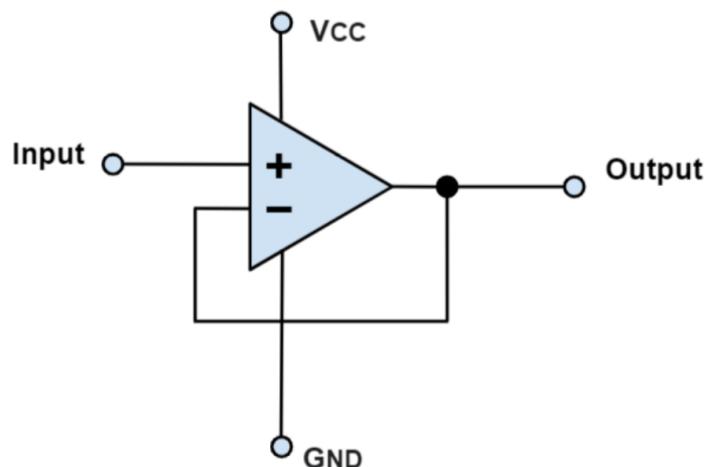


**Figure 1.2:** Voltage Follower

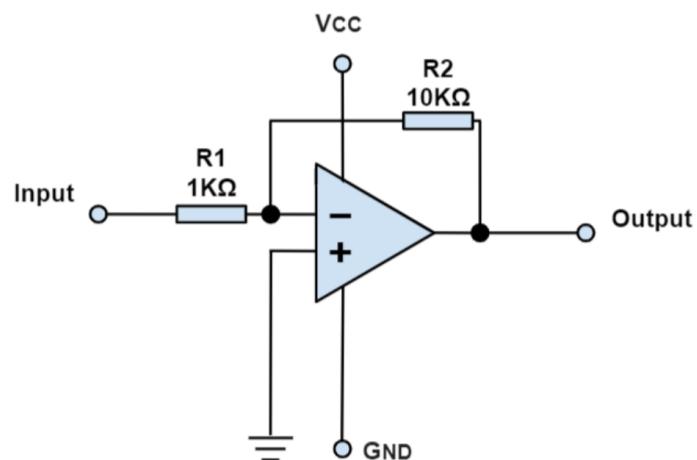


**Figure 1.3:** Inverting Amplifier

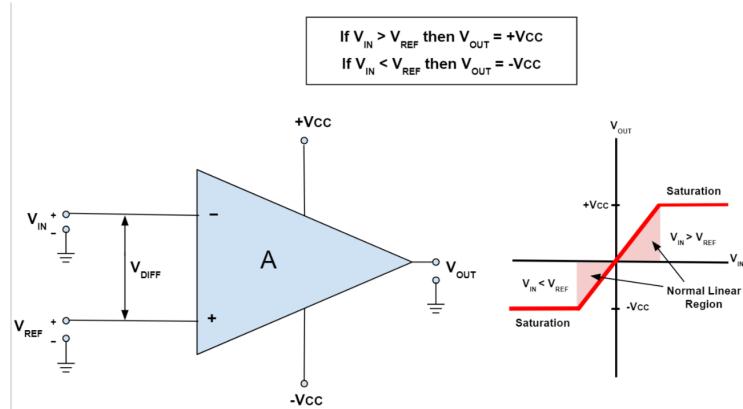

**Figure 1.4:** Voltage Comparator

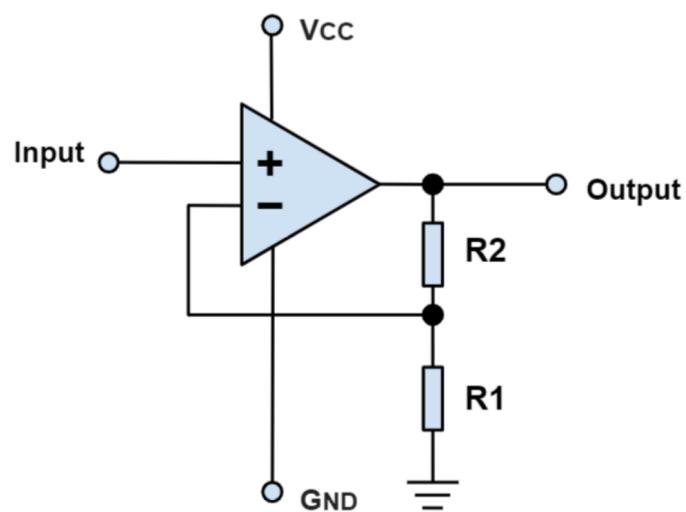

**Figure 1.5:** Non-Inverting Amplifier

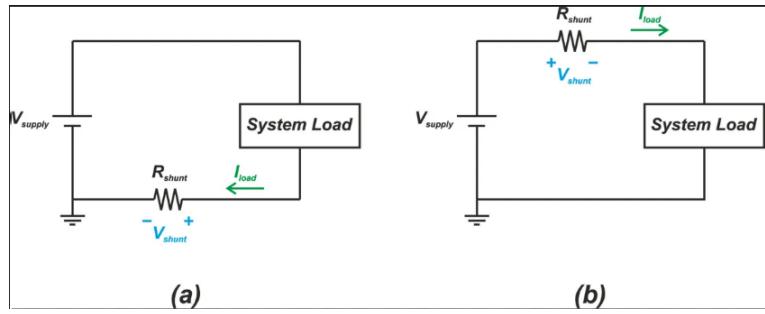

**Figure 1.6:** Lowside vs Highside

	Rogowski coil	Current Transformer	AMR	GMR	Hall effect	Fluxgate	Shunt
<b>Current type</b>	AC	AC	AC and DC	AC and DC	AC and DC	AC and DC	AC and DC
<b>Current range</b>	Medium	High	Medium	Medium	Medium	High	Low
<b>Accuracy</b>	Low	Medium	Medium	Medium	Medium	High	High
<b>Temperature drift</b>	High	Medium	Medium	Medium	Medium	Low	Low
<b>Inherent isolation</b>	Yes	Yes	Yes	Yes	Yes	Yes	No

**Figure 1.7:** Different Current Sensors

## 1.2. Current sensing

### Low Side and High Side Current Sensing

Low side current sensing happens when the sensing resistor is placed below the load. The voltage seen at the current sensing circuit is near ground and therefore uses less power and is safer. This does however make the system ground and supply ground different. The configuration can be shown in Figure 1.6. A high side current sensor configuration is achieved by placing the sensing resistor between the power supply and load. The system then only has one ground however the sensing circuit is more susceptible to fluctuations over the load.

### AC Current Sensing and DC Current Sensing

Certain current sensors and methods of measuring current can only measure AC or DC currents. Different methods are shown in figure 1.7. This needs to be considered when designing for the collision detection.


### Power requirements

It is important to not use too much power when designing the current sensor. By using a low-side current sensor. The dissipated power in the shunt resistor will be less. By using less power, the DC motor will be able to perform better and the vehicle will last longer.

# Chapter 2

## Detail design

The maximum stall current was found to be 1.01 A. This was found by powering the motor and attaching the wheel. By stopping the wheel and observing the current used by the motor when the wheel was not able to move, the maximum current was observed. This was done quickly as stalling the motor for long will destroy the motor. The measurement and setup can be seen in figure 2.1. When the motor was running with no force stopping it, it used about 150mA. However the motor will have to move the entire vehicle and therefor will consume about 200-300mA.

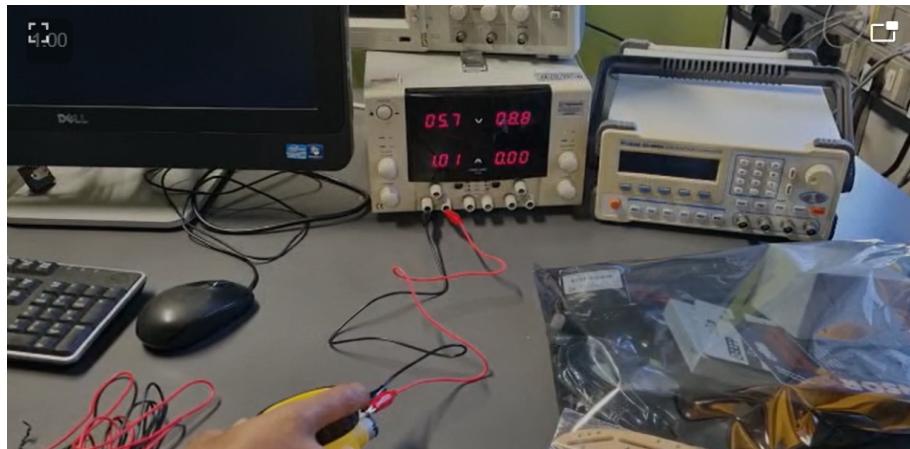

**Figure 2.1:** Stalling Test

Figure 2.2 was taken from Texas instruments. These were the main implementations of a low side current sensor. 2.2a is simpler to build and implement a filter on but is less stable than 2.2b. Due to disturbances on the sensing resistor 2.2b was chosen. If the motor/load affects the current sensor, the effects will be nullified by the extra resistors in 2.2b. The value of R1 was chosen as 250 Ohm. The gain was chosen 300 in order to get a voltage output of over 3Vs. The rest of the resistor values were worked out using the equation in figure 2.2. These values were tweaked in LTSpice in order to get the best output. The max voltage the ESP can read is 3.3V therefor the circuit was designed to be in this range. This can be seen in 2.4

The frequency response was chosen to be around 20 Hz. The following equation was used in order to work out the correct values for the circuit. This was then changed on LTSpice to get a better smoother curve. By smoothing out the graph shown in figure 2.4, the slew rate increased. A value in the middle was chosen. Figure 2.3 is the final design of the circuit. The resistor values were chosen to use less than 150 uA.

$$\frac{1}{2\pi i * f_{sense} * 10 * R2}$$

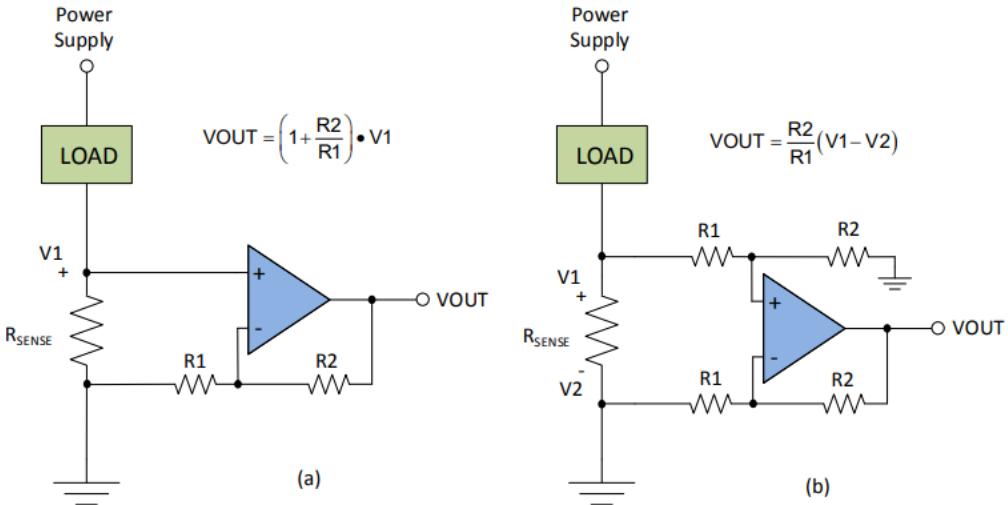


Figure 2.2: Simulation

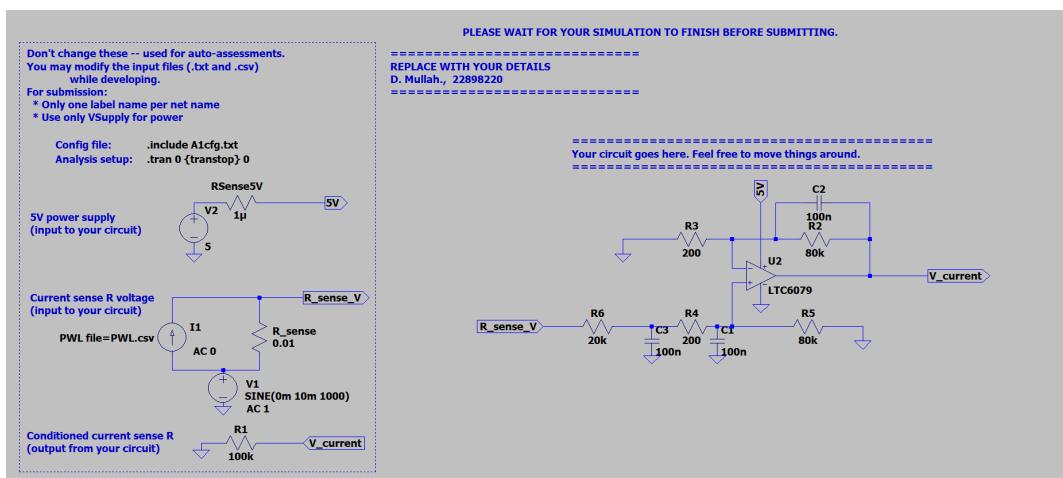


Figure 2.3: Final Design

# Chapter

3

## Results

### 3.1. Current sensor

The simulated result of low side current sensing circuit is shown in figure 3.1. The slew rate and smoothness of the output both meet the requirements. The measured stalling test is shown in figure 2.1 above. The outcome of the stalling test was within the expected range.

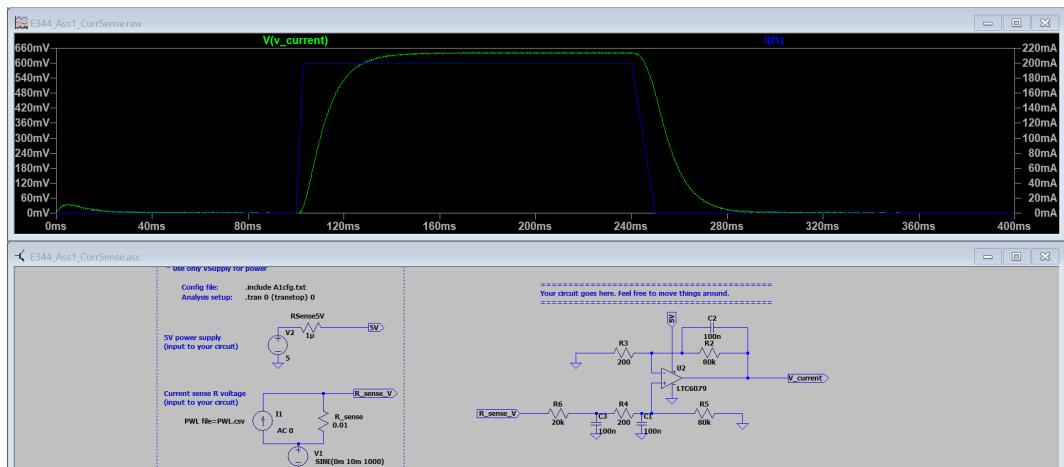


Figure 3.1: Circuit and Output


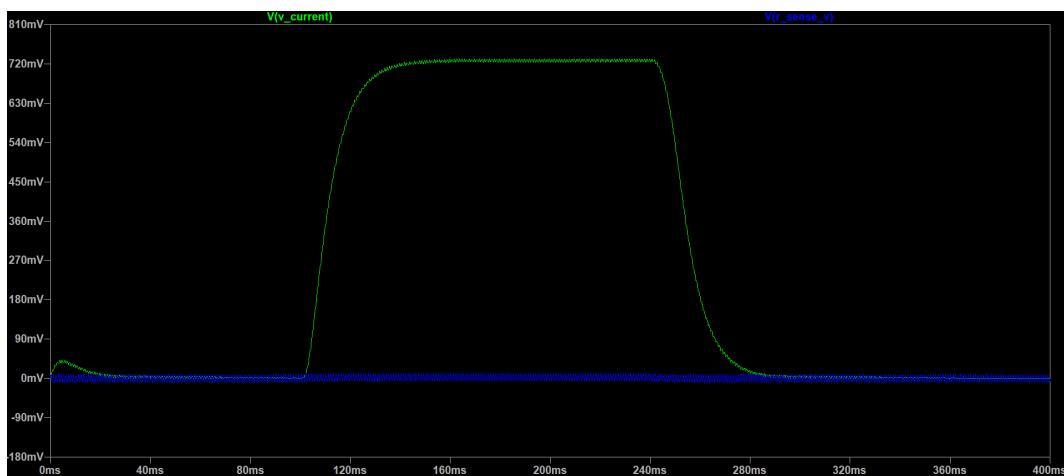



Figure 3.2: Input Vs Output

### 3.2. Current sensor Physical Measurements


The circuit performed well during regular running and when the wheel was stalled. However when the supply current was set to zero the circuit had a voltage output of 0.35V which is above the requirement. This is due to incorrect biasing with the resistor values. The solution would be to add a voltage clipping circuit at the input or recalculate the resistor values. The solution was not implemented due to time and the circuit did respond correctly to all the other specifications.

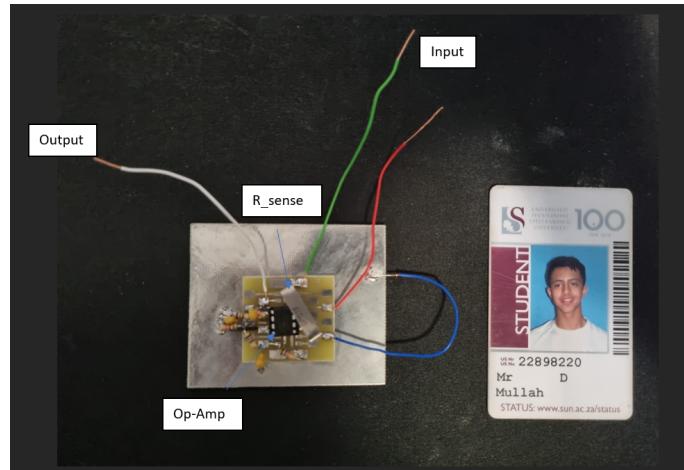

**Figure 3.3:** physical circuit

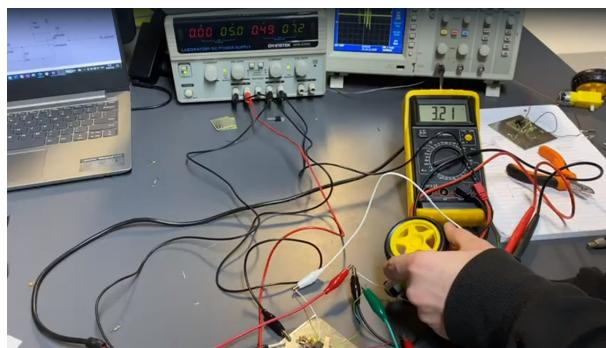

**Figure 3.4:** stalling test

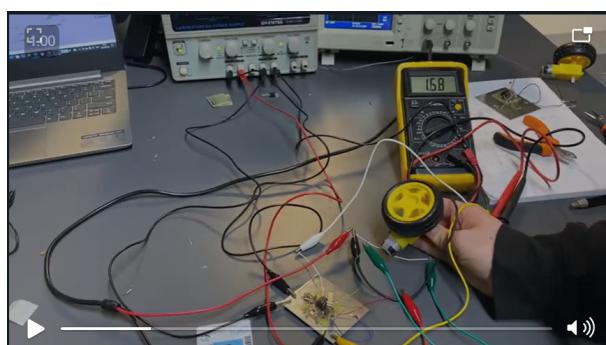

**Figure 3.5:** running test

# **Bibliography**

# Appendix A

## Social contract



UNIVERSITEIT•STELLENBOSCH•UNIVERSITY  
jou kennisvenoot • your knowledge partner

### E-design 344 Social Contract

2022

The purpose of this document is to establish commitment between the student and the organisers of E344. Beyond the commitment made here, it is not binding.

In the months preceding the term, the lecturer (Thinus Booyens) and a few paid helpers (Rita van der Walt, Keegan Hull, and Michael Ritchie) spent countless hours to prepare for E344 to ensure that you get your money's worth, that you are enabled to learn from the module, and demonstrate and be assessed on your skills. We commit to prepare the assignments, to set the assessments fairly, to be reasonably available, and to provide feedback and support as best and fast we can. We will work hard to give you the best opportunity to learn from and pass analogue electronic design E344.

Daanyaal Mullah

I, ..... have registered for E344 of my own volition with the intention to learn of and be assessed on the principals of analogue electronic design. Despite the potential publication online of supplementary videos on specific topics, I acknowledge that I am expected to attend the scheduled lectures to make the most of these appointments and learning opportunities. Moreover, I realise I am expected to spend the additional requisite number of hours on E344 as specified in the yearbook.

I acknowledge that E344 is an important part of my journey to becoming a professional engineer, and that my conduct should be reflective thereof. This includes doing and submitting my own work, working hard, starting on time, and assimilating as much information as possible. It also includes showing respect towards the University's equipment, staff, and their time.

Prof. MJ (Thinus) Booyens

Student number: 22898220

MJ Booyens

Digital signature by MJ Booyens  
Date: 2022-07-02  
13:22:09 +0200

Signature: ..... Signature: .....

Date: 1 July 2022

Date: 31 July 2022

# Appendix

B

## GitHub Activity Heatmap

